

# — MD ITP

By: mdl425  
25-02-2012


[Share](#)

## #5 LAB: LM358 electret microphone preamplifier

### Build LM358 electret microphone preamplifier


("Practical Electronics For Inventors" pages: 537-559)


LM358 Operational Amplifier Data Sheet

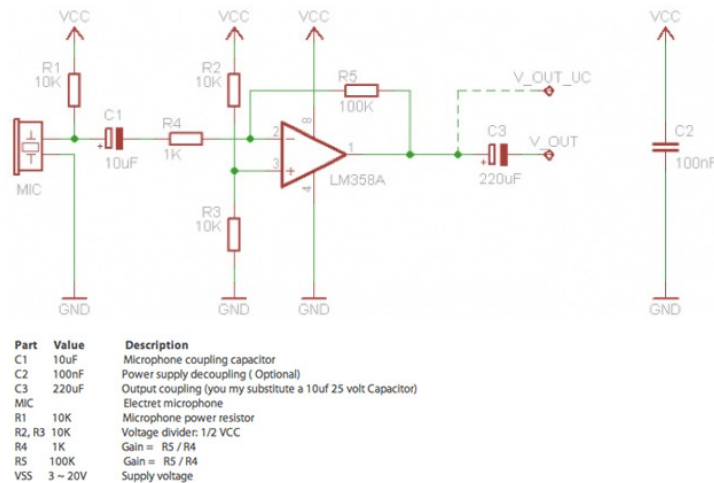
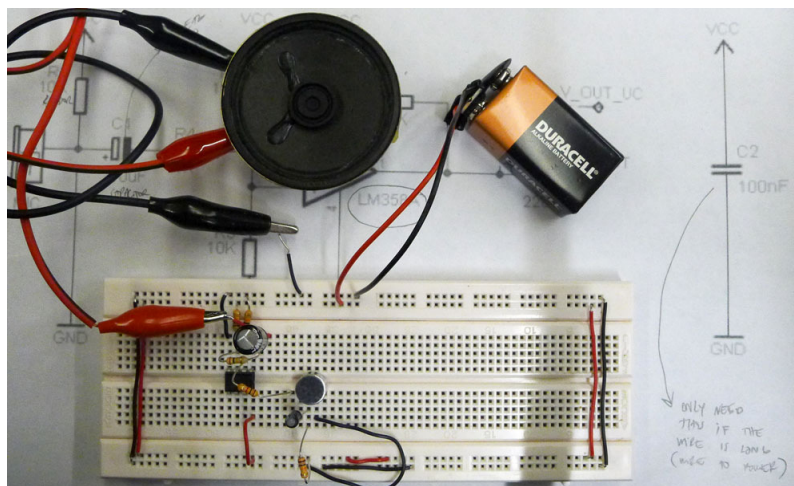
### Categories

Animals, people & those in between  
ANIMATION  
Basic Analog Circuits  
ICM  
Nature of Code  
PCOMP  
Sensor Workshop  
Video & Sound



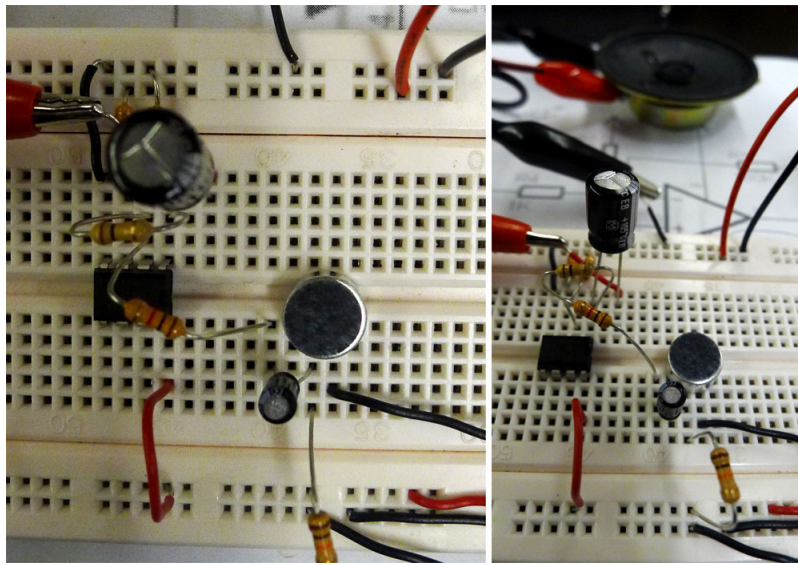

0 comments

Submit yours

Submit comment

Name

Comment

Email

Website

Submit

© 2010 —MD ITP. All Rights Reserved. Powered by Wordpress.

Designed by Wpshower